

# **CPU Architecture**

**LAB4 assignment**

**FPGA based Digital Design**

**Hanan Ribo**

**12.05.2025**

## Table of contents

1.	Aim of the Laboratory .....	3
2.	Assignment definition .....	3
	Performance Test Case .....	3
	Hardware Test Case .....	4
3.	Requirements .....	9
4.	Grading Policy .....	10
5.	References .....	10

## 1. Aim of the Laboratory

- Understanding of digital system synthesis.
- FPGA design as a target HW.

## 2. Assignment definition

In this laboratory you will have to synthesize a Synchronous Digital System based on *LAB1 assignment* for the Cyclone II FPGA with impact on performance and logic usage.

### **Performance Test Case**

In this test case, you must test the performance, area, and functionality of a **digital system**. Generally, Quartus is used to evaluate design timing (as explained in detail in the guidance files on Moodle). To perform timing analysis on a digital system, the design must contain registers that confine the logic paths (explained in guidance files).

**Note: in synchronous digital system this requirement is obeyed inherently.**

In case of pure logic design (for example as ALU), to perform timing analysis, we need to confine the DUT between two synchronous registers (DFF based) operating from the same clock as described in the diagram below to estimate performance.

 


Figure 1 : Test Case in case of pure logic system as ALU

**You must do the following tasks:**

- ModelSim Simulation with maximal coverage (done in LAB1 assignment).
- Quartus Compilation **without** pin assignments and design loading to check the design synthesis performance.
- Find the maximal operating clock  $f_{max}$ , set the clock to constrain the possible maximum value.
- Analyze the logic usage (*based on the compilation report*).
- Analyze the critical path and its location in system. Show the longest (critical) and the shortest paths and explain why.
- Find the frequency limiting operation and explain why it is happening.

**The following must be presented in the report:**

- RTL Viewer results *for each logic block* (of the level underneath top).
- Logic usage for each block (Combinational and Flip-Flops) based on Logic usage report from Quartus II.
- Critical path for each logic block and overall system critical path.
- Optimizations that you have done on the code for the FPGA.

***Hardware Test Case***

In the hardware test case, you will have to test an **ALU digital system** onto D10-Standard FPGA board.


- Board *ten* switches (SW9-SW0) and push *four* debounced pushbuttons (KEY3-KEY0) will be used as *Input interface*.
- Board *ten* red LEDs (LEDR9-LEDR0) and *six* 7-segment displays (HEX5-HEX0) used as *Output interface*.
- Connections between the 2x20 GPIO Expansion Header and Cyclone V SoC FPGA

[Figure 2a: I/O interface of the DE10-Standard FPGA board](#)


[Figure 2b: I/O interface of the DE2-115 FPGA board](#)

**Figure 2 : I/O interface of the DE10-Standard and the DE2-115 FPGA boards**


The digital system is composed of two concurrent parts, combinatorial and synchronous, as shown in Figures 3 and 4.

 

**Figure 3: Digital System subparts**

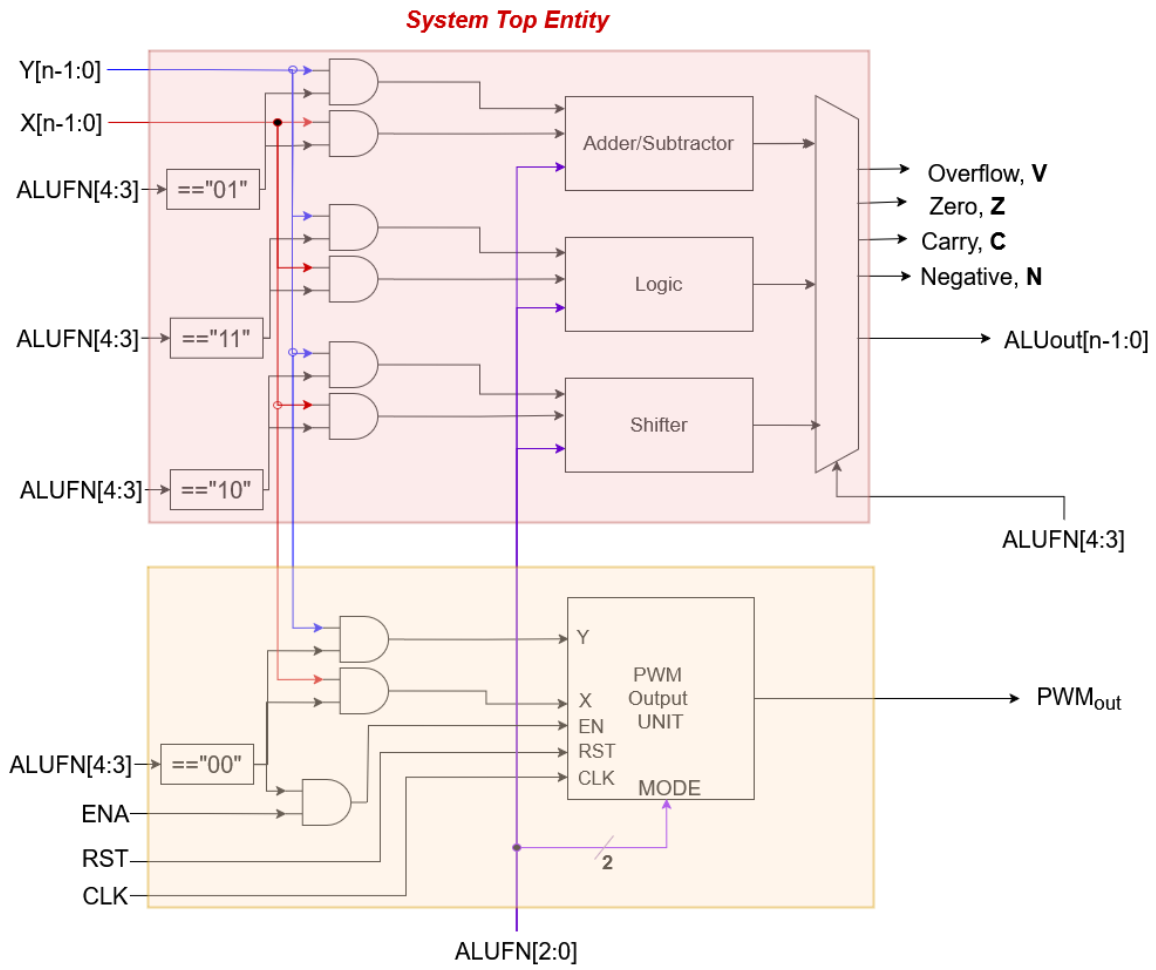

**Figure 4: Digital System subparts architecture**

 

**Figure 5: PWM output unit architecture**

The whole system must be connected to the Altera board interfaces according to the following diagram:


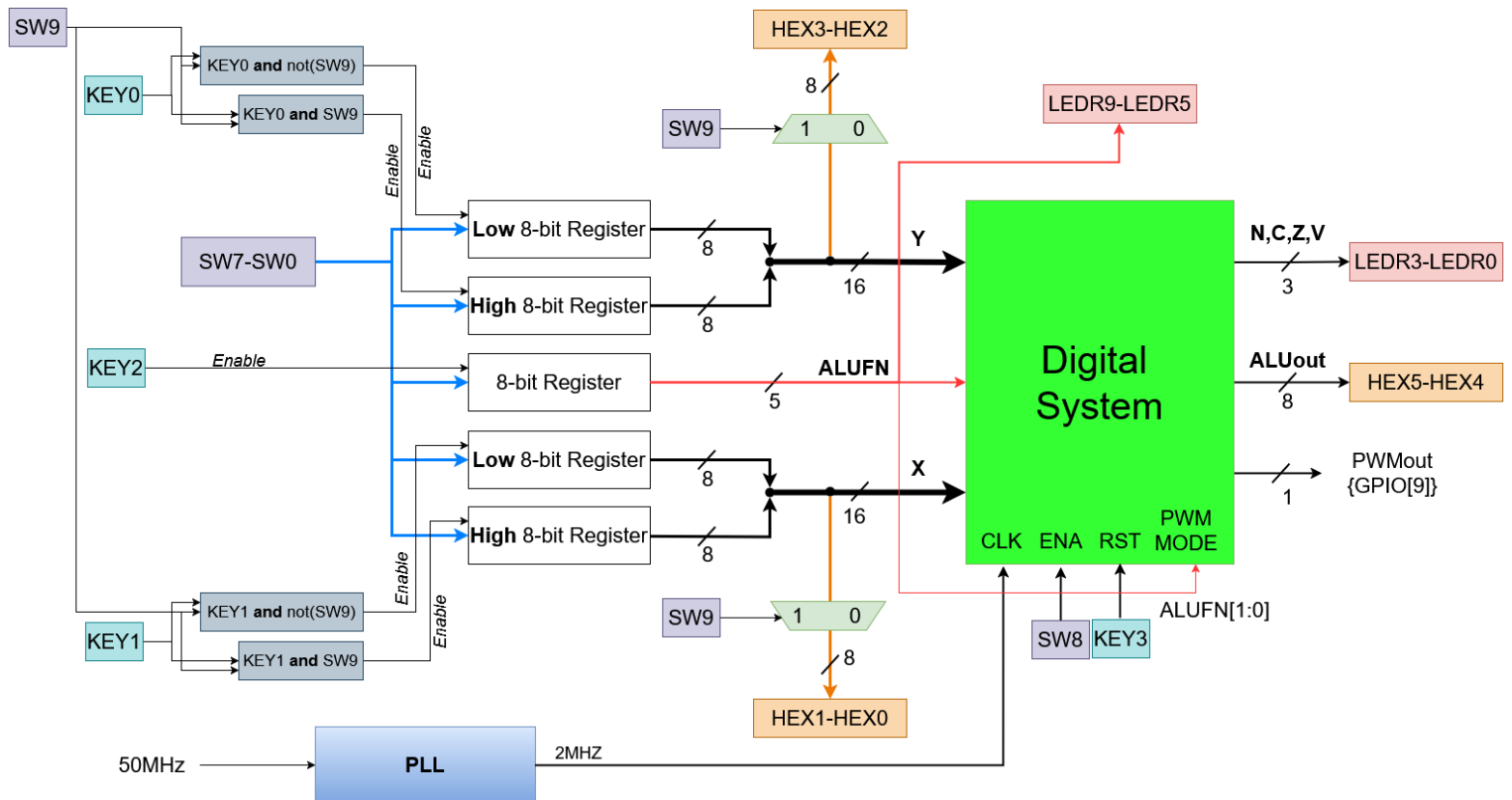


Figure 6: Digital system with I/O interface

The ISA of the combinatorial subpart is given in Figure 7, which is associated with the LAB1 task.

Function Type	Decimal value	ALUFN	Operation	Note
<b>PWM Output</b> ( <i>Y and X are 16-bit width</i> )	0	00000	PWM MODE0	PWM Mode is Set/Reset
	1	00001	PWM MODE1	PWM Mode is Reset/Set
	2	00010	PWM MODE2	PWM Mode is Toggle
<b>Arithmetic</b> ( <i>Y and X are 8-bit width</i> )	8	01000	Res=Y+X	
	9	01001	Res=Y-X	Used also for comparison operation
	10	01010	Res=neg(X)	
	11	01011	Res=Y+1	Increment of Y in one
	12	01100	Res=Y-1	Decrement of Y in one
	13	01101	Res=swap(Y)	Res=(YLSHW, YMSHW)
<b>Shift</b> ( <i>Y and X are 8-bit width</i> )	16	10000	Res=SHL Y,X(k-1 to 0)	Shift Left Y of $q \triangleq X(k-1 \dots 0)$ times Res=Y(n-1-q...0)#(q@0) <b>When <math>k = \log_2 n</math></b>
	17	10001	Res=SHR Y,X(k-1 to 0)	Shift Right Y of $q \triangleq X(k-1 \dots 0)$ times Res=(q@0)#Y(n-1...q) <b>When <math>k = \log_2 n</math></b>
<b>Boolean</b> ( <i>Y and X are 8-bit width</i> )	24	11000	Res=not(Y)	
	25	11001	Res=Y or X	
	26	11010	Res=Y and X	
	27	11011	Res=Y xor X	
	28	11100	Res=Y nor X	
	29	11101	Res=Y nand X	
	30	11110	Res=Y xnor X	

Figure 7: ISA of the combinatorial subpart of digital design

 

### 3. Requirements

1. The report file (LAB4.pdf) content should include page numbers.
2. Images and tables will be numbered. The caption of an image and a table below the image or table. The top-level design must be structural; all other modules can be structural/ behavioral or mixed modeling (structural and behavioral).
3. The behavioral parts of the design (except the test bench) must be synthesized, pay attention to the logic that you are describing.
4. Block diagrams for the behavioral parts of the design that describe the logic behind the behavioral code can be taken from Quartus RTL Viewer
5. The design must be well commented.
6. Elaborated analysis and waveforms:
  - Remove irrelevant signals.
  - Zoom in on regions of interest.
  - Draw clouds on the waveform with explanations of what is happening.
  - Change the waveform colors in ModelSim for clear documentation (*Tools->Edit Preferences->Wave Windows*).
  - Resource Usage from Quartus.
  - **Maximal Frequency and critical paths of the DUT design from the Timing Analyzer (for each subpart, in addition to the whole digital system design)**
  - **Proof of work using Signal Tap is mandatory.**
7. Conclusions
8. A ZIP file in the form of **id1\_id2.zip** (where id1 and id2 are the identification number of the submitters, and  $id1 < id2$ ) *must be upload to Moodle only by student with id1* (any of these rule's violation disqualifies the task submission).
9. The **ZIP** file will contain the next five subdirectories (*only the exact next sub folders*):

Directory	Contains	Comments
VHDL	Project VHDL files	Only VHDL files, excluding test bench <b>Note: your project files must be well compiled (in ModelSim and Quartus separately) without errors as a basic condition before submission</b>
TB	VHDL files that are used for test bench	Only one <b>tb.vhd</b> for the overall DUT
SIM	ModelSim DO files	Only for <b>tb.vhd</b> of the overall DUT
DOC	Project documentation	<b>Readme.txt</b> and <b>Lab4.pdf</b> report file
Quartus	<ul style="list-style-type: none"> <li>Signal Tap files used in project verification (for one Arithmetic and one Shift operations)</li> <li>Project SOF file</li> <li>Project SDC file</li> </ul>	Do not place files that are not relevant for compilation or is a result of compilation

**Table 1: Directory Structure**

## 4. Grading Policy

Weight	Task	Description
10%	Documentation	The "clear" way in which you presented the requirements and the analysis and conclusions on the work you have done.
90%	Analysis and Test	The correct analysis of the system (under the requirements)

**Table 1 : Grading**

Under the above policy, you will be also evaluated using common sense:

- Your files will be compiled and checked; the system must work.
- Your design and architecture must be intelligent, minimal, effective and well organized.

## 5. References

- [1] Altera Cyclone II data book on <http://www.altera.com/literature/lit-cyc2.jsp>  
[2] Quartus II manuals : <http://www.altera.com/support/software/sof-quartus.html>  
[3] DE1 User Manual on <http://hl2.bgu.ac.il – Course Library=>FPGA>  
[4] Cyclone II Technical information <http://www.altera.com/literature/lit-cyc2.jsp>